

IC161P: APPLIED ELECTRONICS

Introductory class Assignment

By Adarsh Santoria(B21176)

1.Abstract

The objective of the experiment is to plot V_{in} and V_{out} graph for the following circuits using LT SPICE and understand the behaviour of the diode.


2.Apparatus Required

S.N.	Name
1	Diode
2	Resistance
3	Capacitor
4	Power Supply
5	Connecting Wires

3.Theory


A Diode is an electronic device made by joining P type and N type semi-conductor which allows the current to flow in one direction that is forward biased. The opposite side which doesn't allow is reverse biased. The P side has holes as its majority charge carriers while N side has electrons as its majority charge carriers.

Diode Symbol

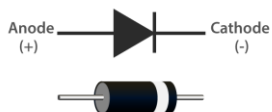


4.Procedure

Experiment-1

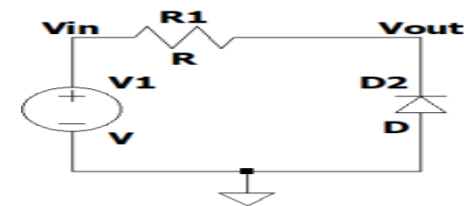


- Take a diode(D1) , a $10k\Omega$ resistance(R) and an AC sinusoidal source(V1) of frequency of 2 MHz and amplitude 5V and connect them by wires as prescribed in circuit above.

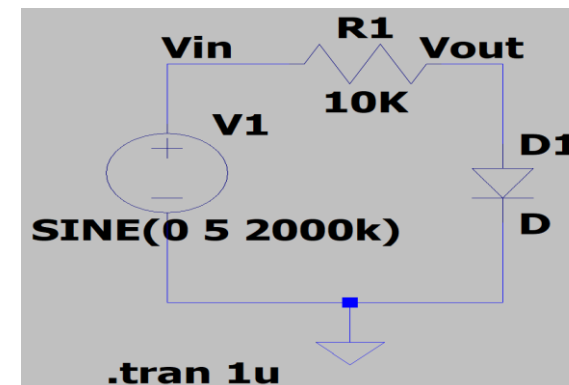
- Label the respective nets as given (V_{in} & V_{out}).



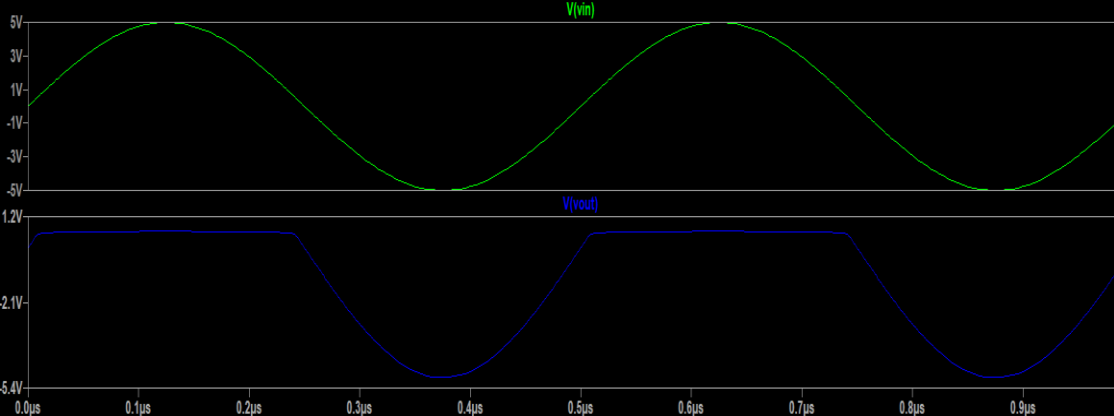- Plot the graphs of voltages at V_{in} and V_{out} .




Experiment-2

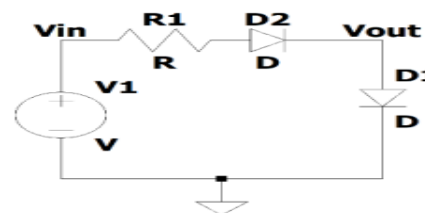


- Take two diode(D1 & D2) ,a 10kΩ resistance(R1) and an AC sinusoidal source(V1) of frequency of 2 MHz and amplitude 5V and connect them by wires as prescribed in circuit above.

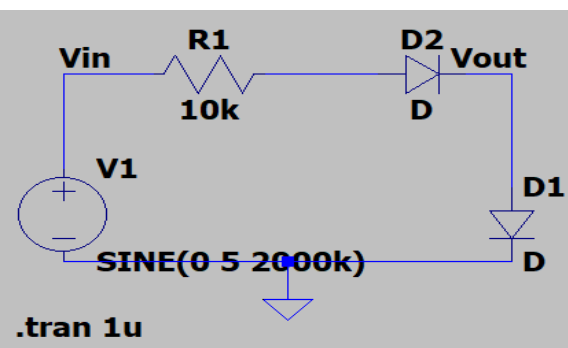
- Label the respective nets as given (Vin & Vout).



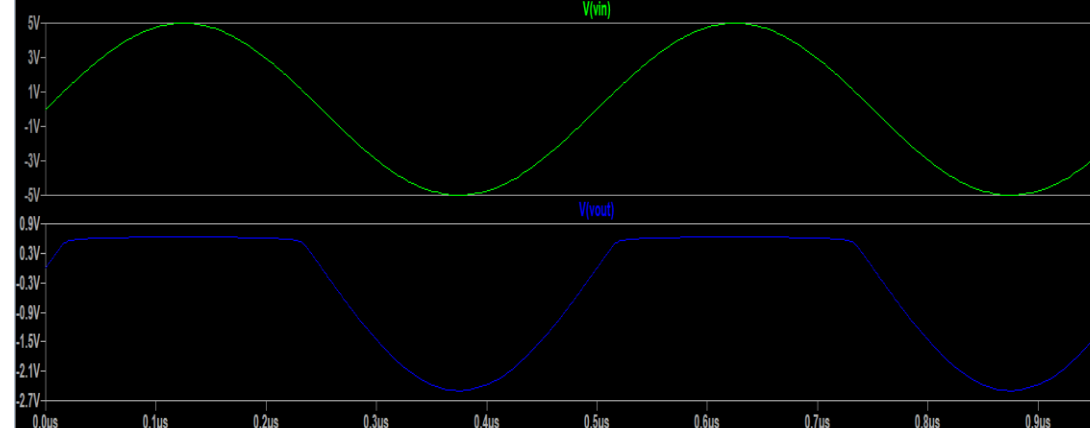- Plot the graphs of voltages at Vin and Vout.




Experiment-3

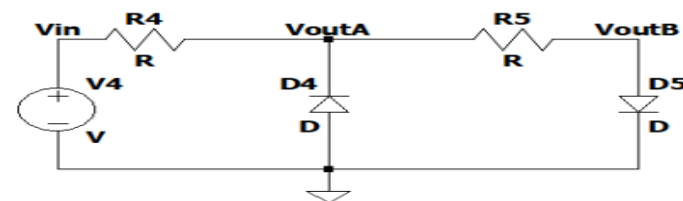


- Take two diode(D4 & D5) ,two 10kΩ resistance(R4 & R5) and an AC sinusoidal source(V4) of frequency of 2 MHz and amplitude 5V and connect them by wires as prescribed in circuit above.

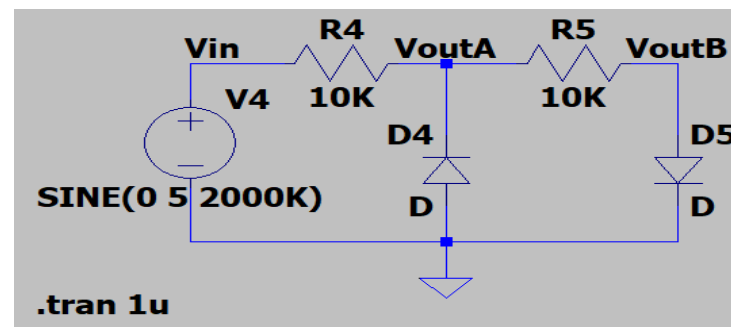
- Label the respective nets as given (Vin, VoutA & VoutB).



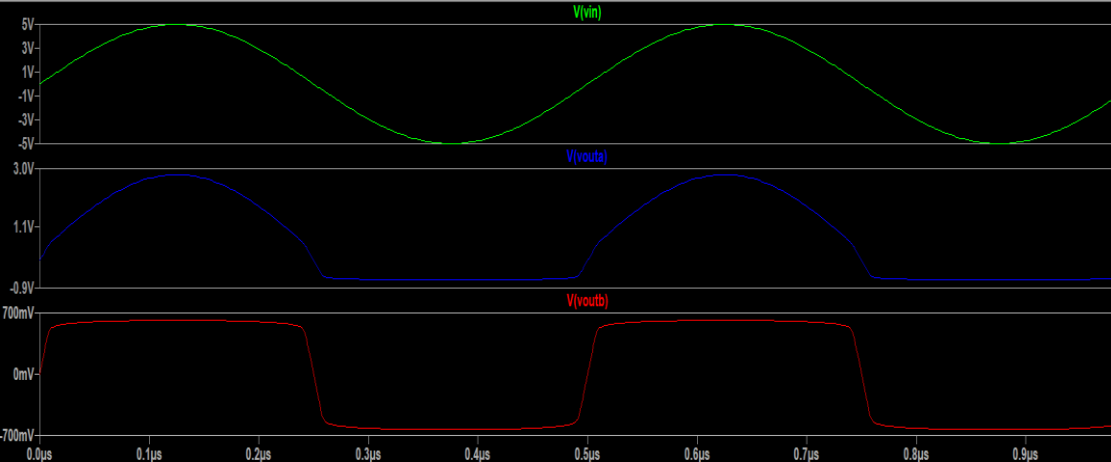- Plot the graphs of voltages at Vin, VoutA & VoutB.




Experiment-4

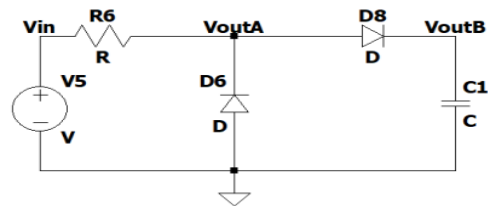


•Take two diode(D6 & D8), a 10k Ω resistance(R6), a 10 μ F capacitor(C1) and an AC sinusoidal source(V5) of frequency of 2 MHz and amplitude 5V and connect them by wires as prescribed in circuit above.

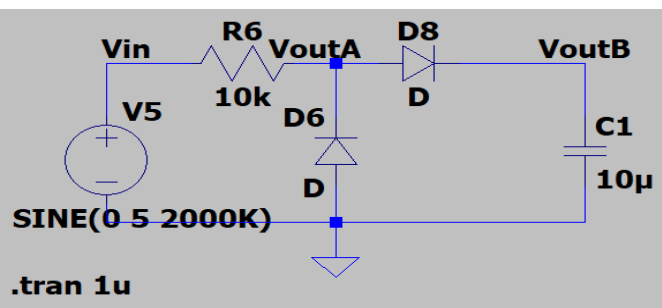•Label the respective nets as given (Vin, VoutA & VoutB).



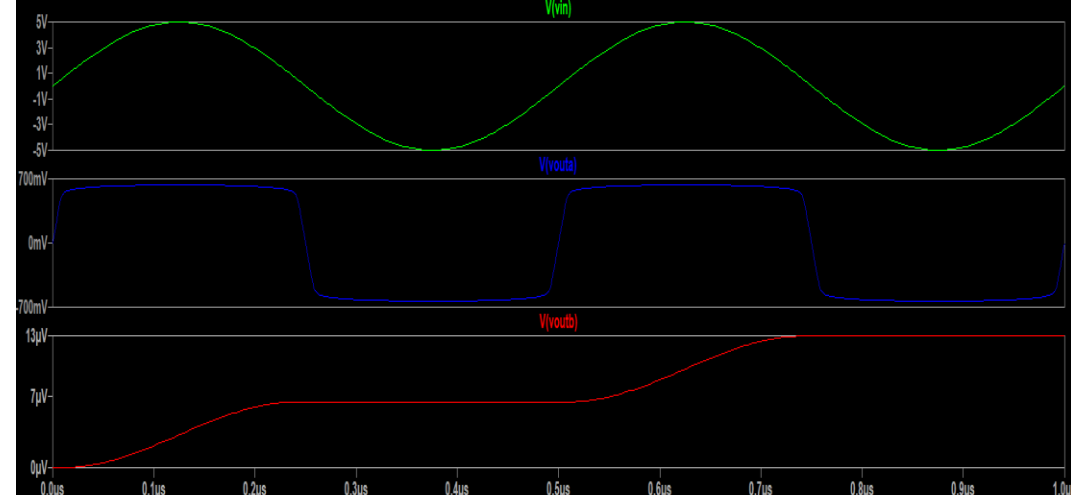•Plot the graphs of voltages at Vin, VoutA & VoutB.



4.Conclusion

In forward biased, the diode starts conducting after a certain voltage called threshold voltage(which is nearly 0.7V) while in reverse biased, it almost has a non-conducting nature.

Something interesting happens in capacitor's case where frequency of time constant of capacitor is much less than the frequency of power source which allows the capacitor to loose a very little charge when voltage is decreasing till the voltage is gained to that point. This results in constant voltage across capacitor after few cycles.