

IC161P-Applied Electronics Lab

Lab Exercise-3. Design of Common Emitter Amplifier

By Adarsh Santoria (B21176) [Group-D]

1. Abstract

To understand the functioning of Common Emitter Amplifier

2. Apparatus Required


S.N.	Devices
1	2N222 Transistor
2	Resistor
3	Voltage Sources
4	Capacitor
5	Connecting Wires

3. Theory

Amplifier is an electronic device which increases the strength of voltage in a circuit.


Common Emitter Amplifier is a type of voltage amplifier which has three BJT(Bipolar Junction Transistor).

Basic NPN common-emitter circuit


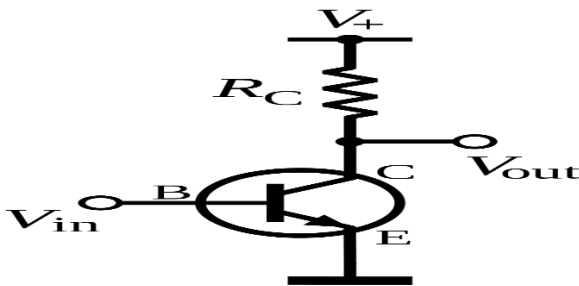


4. Circuit diagram and analysis

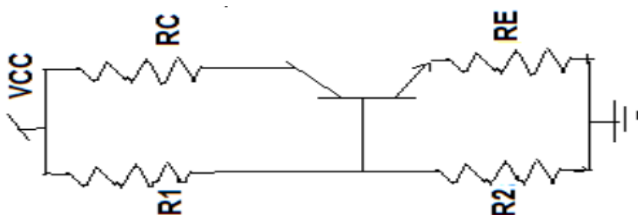
1. Design a common emitter BJT amplifier as shown in figure 1 with $g_{mS} = 19.2$ and $R_E = 400\Omega$. Assume that $V_{RE} = 200\text{mV}$ and $I_{SA} = 15.6734 \times 10^{-6}$. Let the amplifier is designed to have a $\beta = 150$. Assume $V_{CC} = 12\text{V}$.




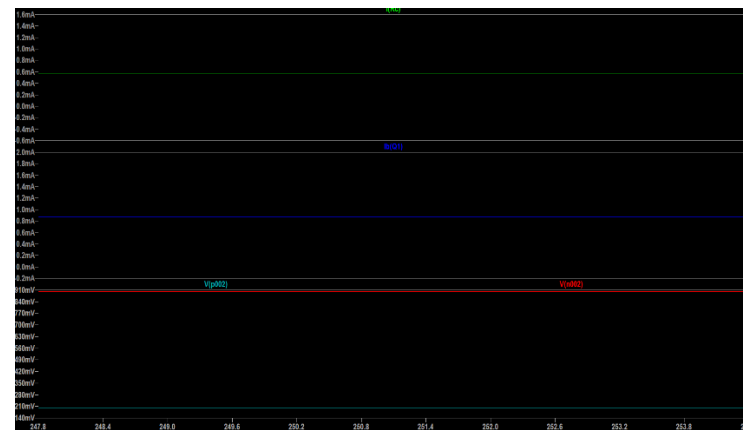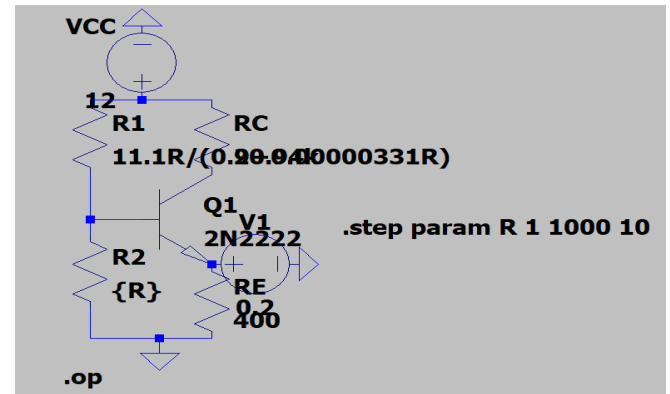A. Estimate the sensitivity of C_I , B_I and V_{BE} to variation in R_2 .



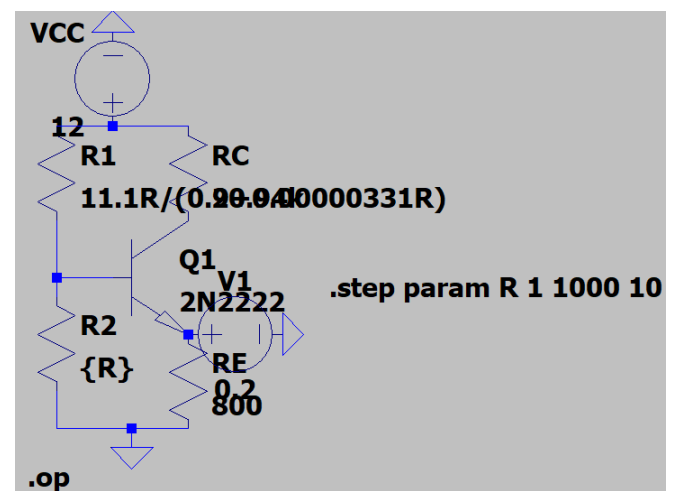B. Now suppose R_E is increased by 400Ω . Once again, estimate the sensitivity of C_I , B_I and V_{BE} to variation in R_2 . What can you infer about the sensitivity of the circuit parameters to variation in R_E ? What happens to the collector emitter potential drop and what will be the potential pitfall if R_E is varied in this manner.




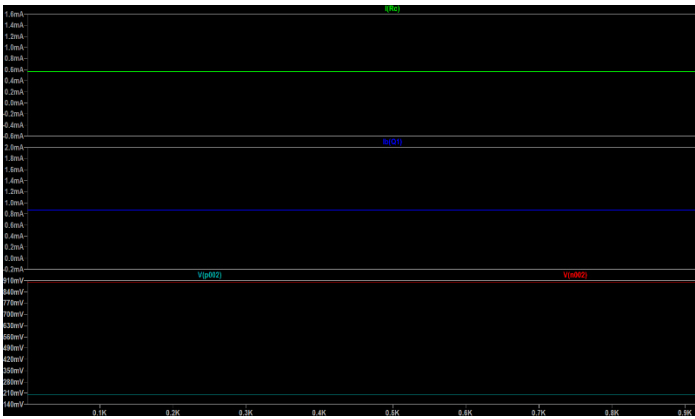


As we can see from above example that we can control AV(voltage gain) and voltages and current at different positions by changing some elements in circuit.

On changing one element, it may change some of mentions or may all depending on how it is related.

On increasing R_E , I_E decreases which causes decrease in current in different wires of circuit and voltages also decreases as a result but V_{RE} remains constant.

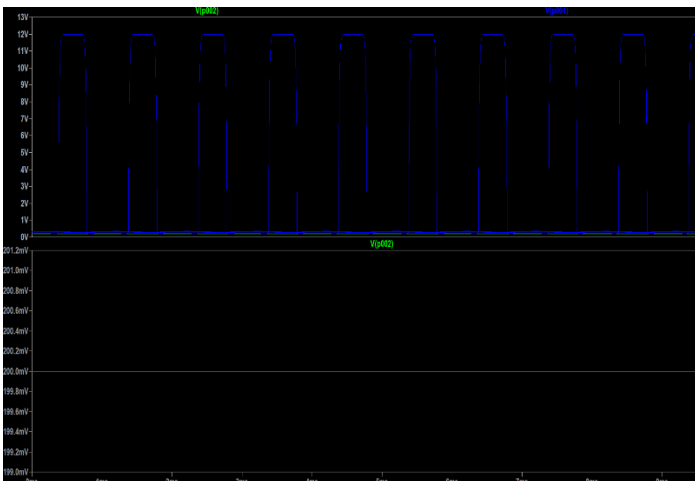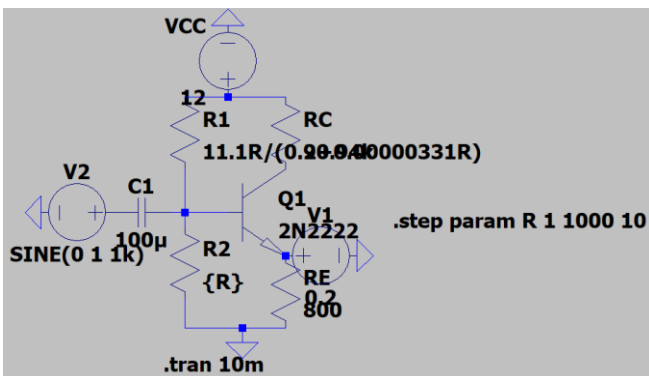C. Now add a small signal of amplitude 1mV and frequency 1KHz to the base. Obtain the timing waveform for input signal V_{in} and V_{out} for 10ms. Choose coupling capacitors of value $100\mu F$.



D. Study the effect of R_E on V_{RE} and voltage gain A_V .

Soln: V_{RE} always remains constant but it changes when R_E is infinity. This is the case when all voltages drop across it.

On increasing V_{RE} , Voltage gain A_V increases and vice-versa.

5.Conclusion